Evaluation Board Report

24V 36W AC-DC power supply

Design Specs	Value	Unit			
Input Voltage	85-265	VAC			
Output Voltage	24	VDC			
Output Current	1.5	Α			
Isolation	YES				
MPS IC	HFC0100HS				
Application	 Battery charger: cellular phone, digital camera, video camera, etc Standby power supply: TV, Desk top PC, Audio system, etc SMPS: printer, DVD, VCR, CD player, STBs, Adapter 				

Document Number	EBXXX
Author	Application Engineering Department
Date	Nov, 2014
Revision	1.0

Design Summary

EVHFC0100HS-00A evaluation board provides a reference design for a universal offline power supply with 24V, 1.5A output. It contains the complete specification of the power supply, a detailed circuit diagram, the entire bill of materials required to build the power supply, drawing of the power inductors and transformers, and test data of the most important performance.



DESCRIPTION

The HFC0100 is a peak current mode controller with Green Mode Operation. Its high efficiency feature over the entire line and load range meets the stringent world-wide energy efficiency requirements.

The HFC0100 integrated with a high voltage current source, its valley detector ensures minimum Drain-Source voltage switching (Quasi-Resonant operation). When the output power falls below a given level, the controller enters the burst mode.

The HFC0100 provides various protections, such as Thermal Shutdown (TSD), Vcc Under Voltage Lockout (UVLO), Over Load Protection (OLP), Over Voltage Protection (OVP) and so on.

The HFC0100 is available in the 8-pin SOIC8 package.

ELECTRICAL SPECIFICATION

Parameter	Symbol	Value	Units
Supply Voltage	VIN	85~265	VAC
Output Voltage	Vouт	24	V
Output Current	l _{оит}	1.5	Α

FEATURES

- Universal Main Input Voltage (85~265VAC)
- Quasi-Resonant Operation
- Valley Switching for high efficiency and EMI
- Burst Mode for low standby consumption
- Internal High Voltage Current Source
- High level of integration, allows a very low number external component count
- Maximum Frequency Limited
- Internal Soft Start
- Internal 250nS Leading Edge Blanking
- Thermal shutdown
- Vcc UVLO with Hysteresis
- Over Voltage Protection
- Over Load Protection.

APPLICATIONS

- Battery charger: cellular phone, digital camera, video camera, etc
- Standby power supply: TV, Desk top PC, Audio system, etc
- SMPS: Inc jet printer, DVD, VCR, CD player, STBs, Adapter for NB


"MPS" and "The Future of Analog IC Technology", are Registered Trademarks of Monolithic Power Systems, Inc..

EVHFC0100HS-00A EVALUATION BOARD



(L x W x H) 12.7cm x 5.4cm x 3.5cm


Board Number	MPS IC Number	
EVHFC0100HS-00A	HFC0100HS	

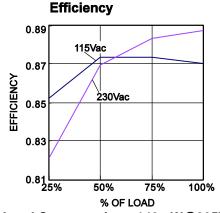

No Load Consumption:<140mW@265Vac



EVALUATION BOARD SCHEMATIC

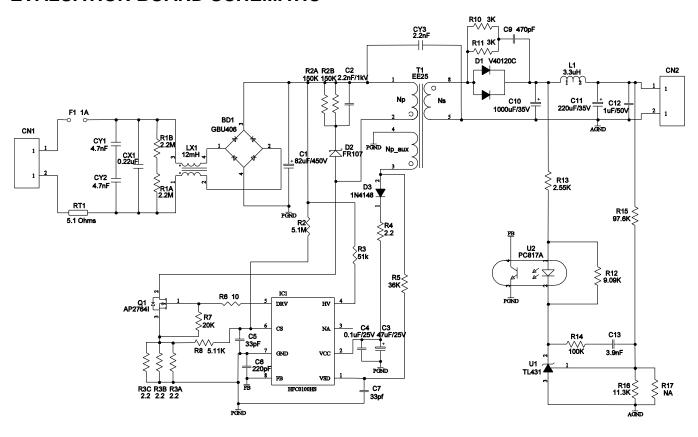

EVHFC0100HS-00A BILL OF MATERIALS

Qty	Ref	Value	Description	Package	Manufacturer	Part Number
1	BD1	GBU406	Bridge Rectifier, 4A/600V	Through Hole	Diodes	GBU406
1	C1	82µF	Electrolytic Capacitor, 450V	DIP	JiangHai	CD266-450V82
1	C10	1000µF	Electrolytic Capacitor, 35V	DIP	Panasonic	1000uF/35V
1	C11	220µF	Electrolytic Capacitor, 35V	DIP	JiangHai	CD287-35V220
1	C12	1µF	Ceramic Cap, 50V, X7R	1206	Murata	GRM21BR71H105KA12L
1	C13	3.9nF	Ceramic Cap, 50V, X7R	0603	Murata	GRM188R71H392KA01D
1	C2	2.2nF	Film Cap, 1000V	DIP		
1	C3	47µF	Electrolytic Capacitor, 25V	DIP	JiangHai	CD28L-25V47
1	C4	0.1µF	Ceramic Cap, 50V, X7R	0603	Murata	GRM188R71H104KA93D
2	C5,C7	33pF	Ceramic Cap, 50V, C0G	0603	Murata	GRM1885C1H330JA01
1	C6	220pF	Ceramic Cap, 50V, X7R	0603	Murata	GRM188R71H221KA01D



EVHFC0100HS-00A BILL OF MATERIALS (continued)

Qty	Ref	Value	Description	Package	Manufacturer	Part Number
1	C9	470pF	Film Cap, 1000V	DIP		
2	CN1, CN2		CONNECTOR-2PINS	Through Hole		
1	CX1	0.22µF	Film CAP, 275V, X2	DIP	Vishay	BFC33920224
2	CY1, CY2	4.7nF	Film CAP, 300V, Y2	DIP	Vishay	VY2472M49Y5US63V7
1	CY3	2.2nF	Film CAP, 500V, Y1	DIP	Vishay	VY1222M47Y5UQ63V0
1	D1	V40120C	Schottky Diode, 40A/120V	TO220A B	·	
1	D2	FR107	Diode, 1A/1000V	DO-41		FR107
1	D3	1N4148	Diode, 0.15A/75V	SOD-123	Diodes	1N4148
1	F1	1A	Fuse, 250V	AXIAL	Cooper Bussmann	SS-5-1A
1	IC1	HFC0100HS	QR controller	SOIC8	MPS	HFC0100HS
1	L1	3.3µH	Inductor, 3A	DIP		
1	LX1	12mH	Common filter	DIP		
1	Q1	AP2764I-A	MOSFET, 650V	TO220	APEC	AP2764I-A
2	R10, R11	3kΩ	Film Res., 1%	1206	Yageo	RC1206FR-073KL
1	R12	9.09kΩ	Film Res., 1%	0603	Yageo	RC0603FR-073K09L
1	R13	2.55kΩ	Film Res., 1%	0603	Yageo	RC0603FR-072K55L
1	R14	100kΩ	Film Res., 1%	0603	Yageo	RC0603FR-07100KL
1	R15	97.6kΩ	Film Res., 1%	0603	Yageo	RC0603FR-0797K6L
1	R16	11.3kΩ	Film Res., 1%	0603	Yageo	RC0603FR-0711K3L
1	R17		Don't Stuff	0603		
2	R1A, R1B	2.2ΜΩ	Film Res., 1%	1206	Royalohm	1206J0225T5E
2	R2A, R2B	150kΩ	Res. 1W	AXIAL		
1	R3	51kΩ	Res.0.25W	AXIAL		
4	R3A, R3B, R3C, R4	2.2Ω	Film Res., 1%	1206	Royalohm	1206F220KT5E
1	R5	36kΩ	Film Res., 1%	1206		1206F3602T5E
1	R6	10Ω	Film Res., 5%	AXIAL		
1	R7	20kΩ	Film Res., 1%	0603	Yageo	RC0603FR-0720KL
1	R8	5.11kΩ	Film Res., 1%	0603	Yageo	RC0603FR-075K11L
1	R2	5.1ΜΩ	Film Res., 5%	1206	Yageo	RI1206L515JT
1	RT1	5.1Ω	NTC	Through Hole	Murata	NTPAA5R1LDNB0
1	T1	84:14:8	Transformer, EF25	Through Hole	_	EF25
1	U1	TL431K	Shunt Regulator	SOT-23	UNISONIC	TL431K
1	U2	PC817A	Photocouple	DIP	YiGuang	PC817A



PRINTED CIRCUIT BOARD LAYOUT

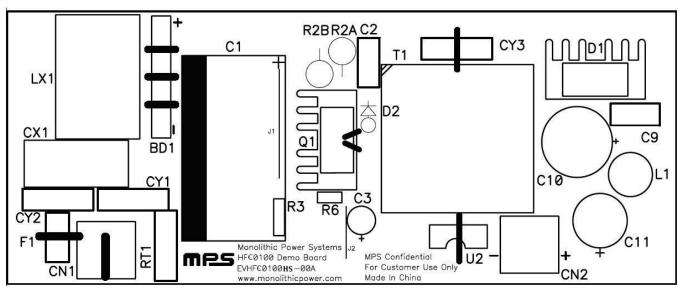


Figure 1 — Top Silk Layer

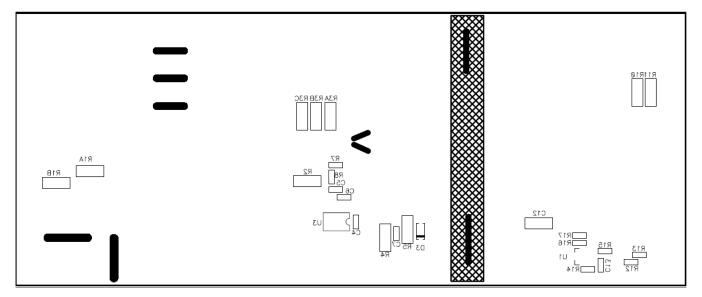


Figure 2 — Bottom Silk Layer



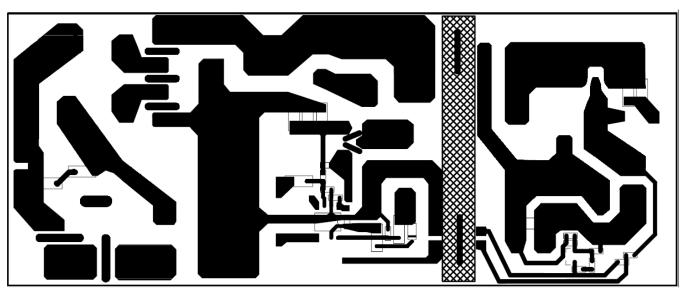


Figure 3 — Bottom Layer



QUICK START GUIDE

- 1. Connect the positive and negative terminals of the load to CN2 port,
- 2. Connect the Line and Neutral terminals of the power supply output to CN1 port.
- 3. Turn the power supply on, the board automatically starts up.

Contact Information

To request this evaluation board, please refer to your local sales offices which can be found from: http://www.monolithicpower.com/Company/Contact-Us

Disclaimer

Monolithic Power Systems (MPS) reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. MPS makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

MPS cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a MPS product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

MPS PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICALAPPLICATIONS.

Inclusion of MPS products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to MPS.

MPS semiconductors are typically used in power supplies in which high voltages are present during operation. High voltage safety precautions should be observed in design and operation to minimize the chance of injury.

NOTICE: The information in this document is subject to change without notice. Please contact MPS for current specifications. Users should warrant and guarantee that third party Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.